

Міністерство освіти і науки України  
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 2

з дисципліни «Моделювання комп'ютерних систем»  
на тему:

«Структурний опис цифрового автомата Перевірка роботи автомата за  
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №14

Виконав:  
ст. гр. КІ-201  
Когут Д.А.  
Прийняв:  
ст. викладач  
каф. ЕОМ  
Козак Н. Б.

Львів 2024

**Мета роботи:** На базі стенда реалізувати цифровий автомат світлових ефектів.

Згідно мого варіанту(2) потрібно реалізувати такі комбінації:

Стан#	LED_0	LED_1	LED_2	LED_3	LED_4	LED_5	LED_6	LED_7
0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0
2	1	1	1	0	0	0	0	0
3	1	1	1	1	0	0	0	0
4	1	1	1	1	1	0	0	0
5	1	1	1	1	1	1	0	0
6	1	1	1	1	1	1	1	0
7	1	1	1	1	1	1	1	1

Та дотримуватися таких вимог:

- Пристрій повинен використовувати тактовий сигнал від мікроконтролера і знижувати частоту за допомогою внутрішнього подільника. Мікроконтролер є частиною стенда Elbert V2 – Spartan 3A FPGA. Тактовий сигнал заведено на вхід LOC P129 FPGA
- Інтерфейс пристрою повинен мати вхід синхронного скидання (RESET)
- Інтерфейс пристрою повинен мати вхід керування режимом роботи (MODE):
  - Якщо MODE = 0 то стан пристрою інкрементується по зростаючому фронту тактового сигналу пам'яті станів.
  - Якщо MODE = 1 то стан пристрою декрементується по зростаючому фронту тактового сигналу пам'яті станів.
- Інтерфейс пристрою повинен мати однорозрядний вхід керування швидкістю роботи (SPEED):
  - Якщо SPEED = 0 то автомат працює зі швидкістю визначеною за замовчуванням
  - Якщо SPEED = 1 то автомат працює зі швидкістю В 2 РАЗИ НИЖЧОЮ ніж в режимі (SPEED = 0)
- Для керування сигналом MODE використати будь який з перемикачів
- Для керування сигналами RESET/SPEED використати будь які з кнопок

## Виконання роботи:

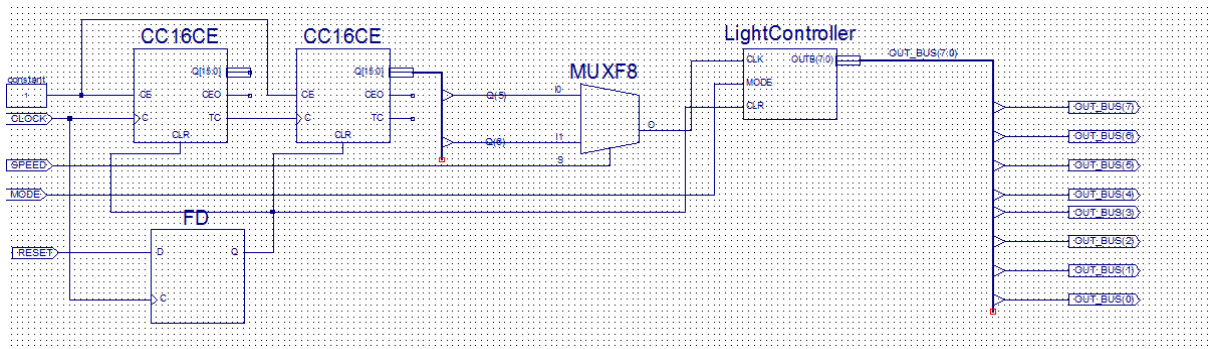


Рис. 1 – Top Level

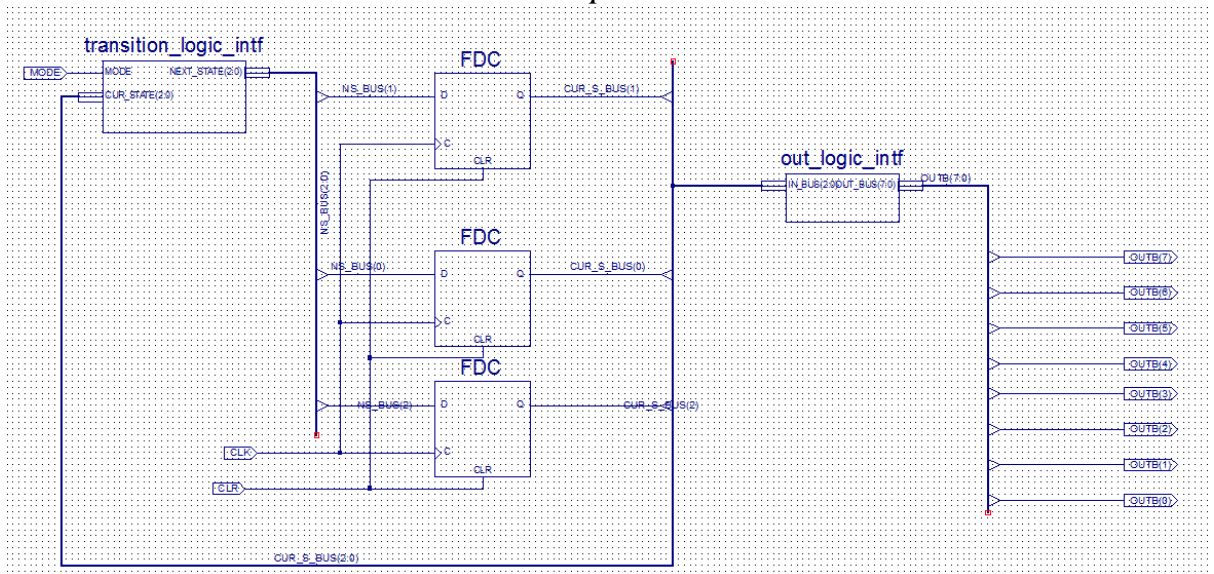


Рис. 2 – Light Controller

Файл TransitionLogic.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity transition_logic_intf is
    Port ( CUR_STATE : in std_logic_vector(2 downto 0);
          MODE : in std_logic;
```

```

        NEXT_STATE : out std_logic_vector(2 downto 0)
            );
end transition_logic_intf;

architecture transition_logic_arch of transition_logic_intf is

begin

    NEXT_STATE(0) <= ((not CUR_STATE(2) and not CUR_STATE(1)
and not CUR_STATE(0)) or
                    (not CUR_STATE(2) and
CUR_STATE(1) and not CUR_STATE(0)) or
                    (CUR_STATE(2) and not
CUR_STATE(1) and not CUR_STATE(0)) or
                    (CUR_STATE(2) and
CUR_STATE(1) and not CUR_STATE(0))) after 1ns;

    NEXT_STATE(1) <= ((not MODE and not CUR_STATE(2) and not
CUR_STATE(1) and CUR_STATE(0)) or
                    (not MODE and not
CUR_STATE(2) and CUR_STATE(1) and not CUR_STATE(0)) or
                    (not MODE and CUR_STATE(2)
and not CUR_STATE(1) and CUR_STATE(0)) or
                    (not MODE and CUR_STATE(2)
and CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and not CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and CUR_STATE(2)
and CUR_STATE(1) and CUR_STATE(0)) or
                    (MODE and CUR_STATE(2)
and not CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and CUR_STATE(1) and CUR_STATE(0))) after 1ns;

    NEXT_STATE(2) <= ((not MODE and not CUR_STATE(2) and
CUR_STATE(1) and CUR_STATE(0)) or
                    (not MODE and CUR_STATE(2)
and not CUR_STATE(1) and not CUR_STATE(0)) or
                    (not MODE and CUR_STATE(2)
and not CUR_STATE(1) and CUR_STATE(0)) or
                    (not MODE and CUR_STATE(2)
and CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and not CUR_STATE(1) and not CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and not CUR_STATE(1) and CUR_STATE(0)) or
                    (MODE and not CUR_STATE(2)
and CUR_STATE(1) and CUR_STATE(0))) after 1ns;

```

```

(MODE and not CUR_STATE(2)
and not CUR_STATE(1) and not CUR_STATE(0)) or
(MODE and CUR_STATE(2)
and CUR_STATE(1) and CUR_STATE(0)) or
(MODE and CUR_STATE(2)
and CUR_STATE(1) and not CUR_STATE(0)) or
(MODE and CUR_STATE(2)
and not CUR_STATE(1) and CUR_STATE(0))) after 1ns;
end transition_logic_arch;

```

Файл OutputLogic.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```
entity out_logic_intf is
```

```

    Port ( IN_BUS : in  std_logic_vector(2 downto 0);
          OUT_BUS : out std_logic_vector(7 downto 0)
          );

```

```
end out_logic_intf;
```

```
architecture out_logic_arch of out_logic_intf is
```

```
begin
```

```

    OUT_BUS(0) <= '1';
    OUT_BUS(1) <= not (not IN_BUS(2) and not IN_BUS(1) and not
IN_BUS(0)) after 1ns;
    OUT_BUS(2) <= not (not IN_BUS(2) and not IN_BUS(1)) after 1ns;
    OUT_BUS(3) <= not ((not IN_BUS(2) and not IN_BUS(1)) or (not
IN_BUS(2) and IN_BUS(1) and not IN_BUS(0))) after 1ns;
    OUT_BUS(4) <= IN_BUS(2) after 1ns;
    OUT_BUS(5) <= ((IN_BUS(2) and IN_BUS(1)) or (IN_BUS(2) and
not IN_BUS(1) and IN_BUS(0))) after 1ns;
    OUT_BUS(6) <= (IN_BUS(2) and IN_BUS(1)) after 1ns;

```

```

OUT_BUS(7) <= (IN_BUS(2) and IN_BUS(1) and IN_BUS(0)) after
1ns;
end out_logic_arch;

```

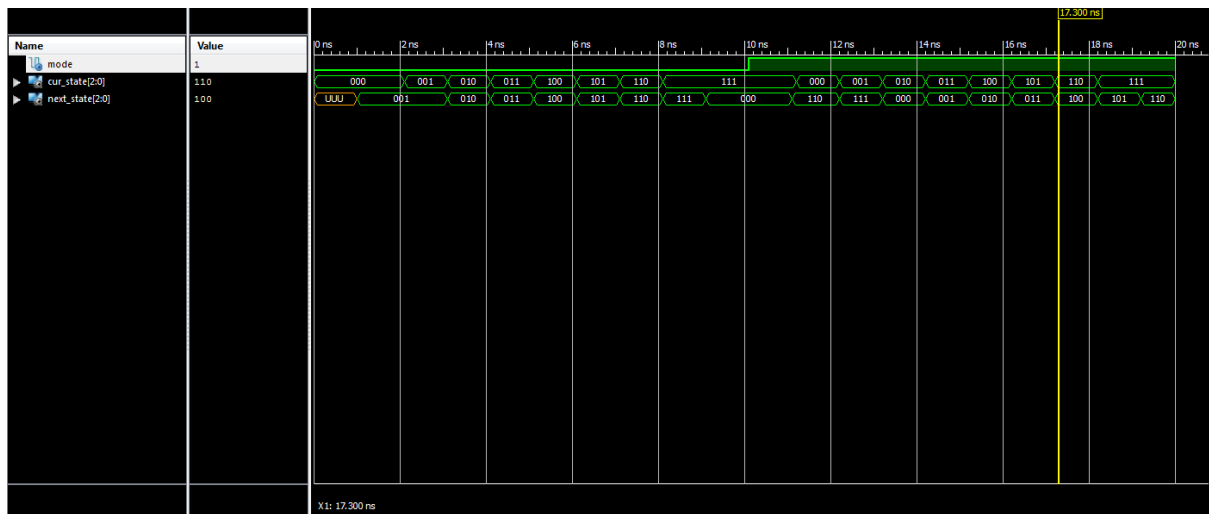


Рис. 3 – Часова діаграма TransitionLogic

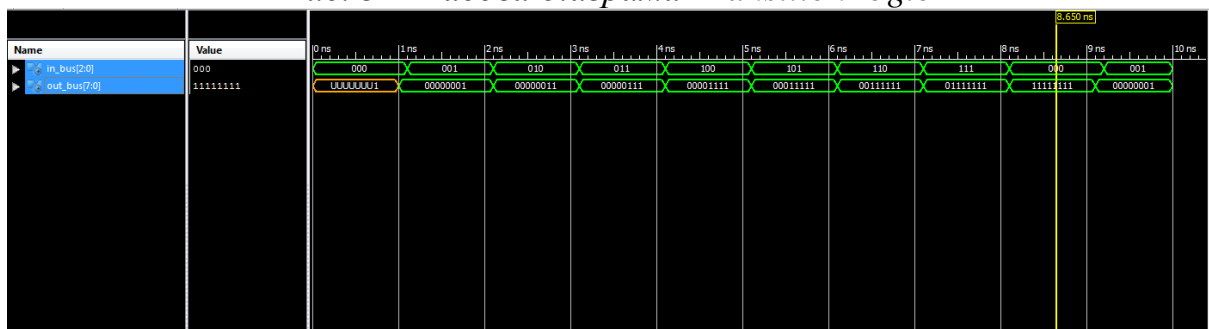


Рис. 4 – Часова діаграма OutputLogic

 


Рис. 5 – Часова діаграма LightController

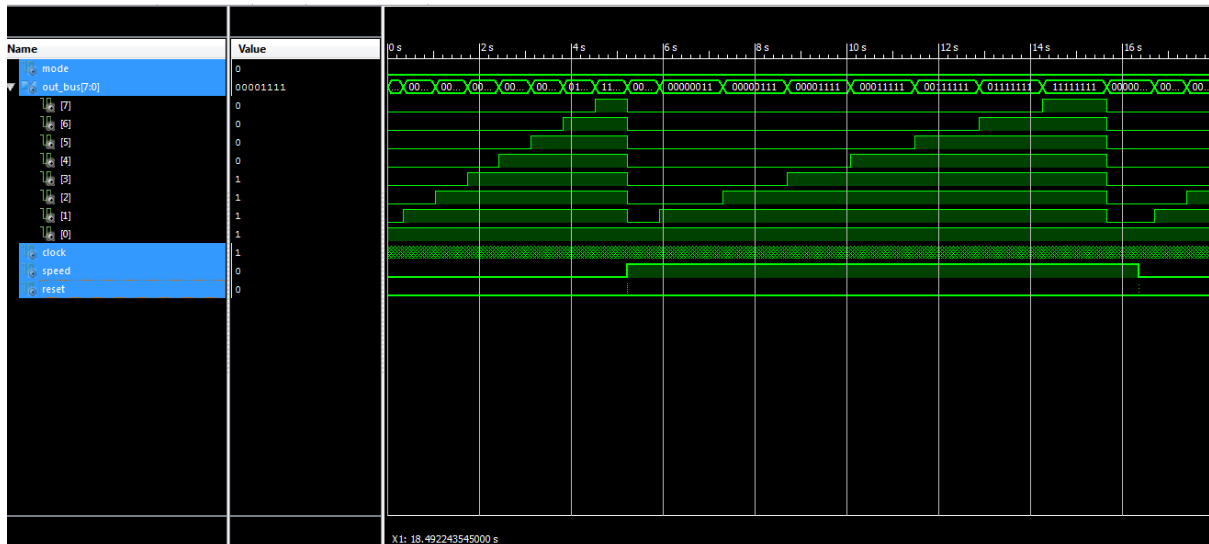


Рис 6. – Часова діаграма TopLevel

Файл TestBechTopLevel.vsd

LIBRARY ieee;

USE ieee.std\_logic\_1164.ALL;

USE ieee.numeric\_std.ALL;

LIBRARY UNISIM;

USE UNISIM.Vcomponents.ALL;

ENTITY TopLevel\_TopLevel\_sch\_tb IS

END TopLevel\_TopLevel\_sch\_tb;

ARCHITECTURE behavioral OF TopLevel\_TopLevel\_sch\_tb IS

COMPONENT TopLevel

PORT( MODE : IN STD\_LOGIC;

OUT\_BUS : OUT STD\_LOGIC\_VECTOR (7 DOWNT0 0);

CLOCK : IN STD\_LOGIC;

SPEED : IN STD\_LOGIC;

RESET : IN STD\_LOGIC);

END COMPONENT;

SIGNAL MODE : STD\_LOGIC;

SIGNAL OUT\_BUS : STD\_LOGIC\_VECTOR (7 DOWNT0 0);

SIGNAL CLOCK : STD\_LOGIC := '0';

SIGNAL SPEED : STD\_LOGIC;

SIGNAL RESET : STD\_LOGIC;

BEGIN

CLOCK <= not CLOCK after 83ns;

UUT: TopLevel PORT MAP(

MODE => MODE,

OUT\_BUS => OUT\_BUS,

```

        CLOCK => CLOCK,
        SPEED => SPEED,
        RESET => RESET
    );

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    MODE <= '0';
    SPEED <= '0';
    RESET <= '1', '0' after 1ms;
    wait until RESET = '0';
    wait for 2ns;
    assert OUT_BUS = "00000001";
    wait for 348128us;
    assert OUT_BUS = "00000011";
    wait for 696255us;
    assert OUT_BUS = "00000111";
    wait for 696255us;
    assert OUT_BUS = "00001111";
    wait for 696255us;
    assert OUT_BUS = "00011111";
    wait for 696255us;
    assert OUT_BUS = "00111111";
    wait for 696255us;
    assert OUT_BUS = "01111111";
    wait for 696255us;
    assert OUT_BUS = "11111111";
    wait for 696255us;
    SPEED <= '1';
    RESET <= '1', '0' after 1ms;
    wait until RESET = '0';
    wait for 2ms;
    assert OUT_BUS = "00000001";
    wait for 1392509us;
    assert OUT_BUS = "00000011";
    wait for 1392509us;
    assert OUT_BUS = "00000111";
    wait for 1392509us;
    assert OUT_BUS = "00001111";
    wait for 1392509us;
    assert OUT_BUS = "00011111";
    wait for 1392509us;

```



```
    assert OUT_BUS = "00111111";  
    wait for 1392509us;  
    assert OUT_BUS = "01111111";  
    wait for 1392509us;  
    assert OUT_BUS = "11111111";  
    wait for 1392509us;  
    SPEED <= '0';  
    RESET <= '1', '0' after 167ns;  
    wait until RESET = '0';  
END PROCESS;  
-- *** End Test Bench - User Defined Section ***  
  
END;
```

**Висновок:** Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат світлових ефектів використовуючи засоби VHDL.